





Tanta University

Faculty of Engineering



Electrical Power and Machines Engineering Department



First Year – Second Term

(Electrical Power and Machines Engineering Department)

Course Title

Electrical Circuits (2)

EPM1203

(3+2)

Dr. Said M. Allam



Part 2

Balanced Three-Phase Circuits





Lecture Outlines

- ☐ Generating Single-Phase Voltage
- ☐ Generating three-phase Voltages
- ☐ Importance of Three-Phase System
- ☐ Three-Phase Generator
- ☐ Basic Three-Phase Circuit
- ☐ Y-Y Three-Phase System
- ☐ Solved Example on Y-Y System



Generating Single-Phase Voltage

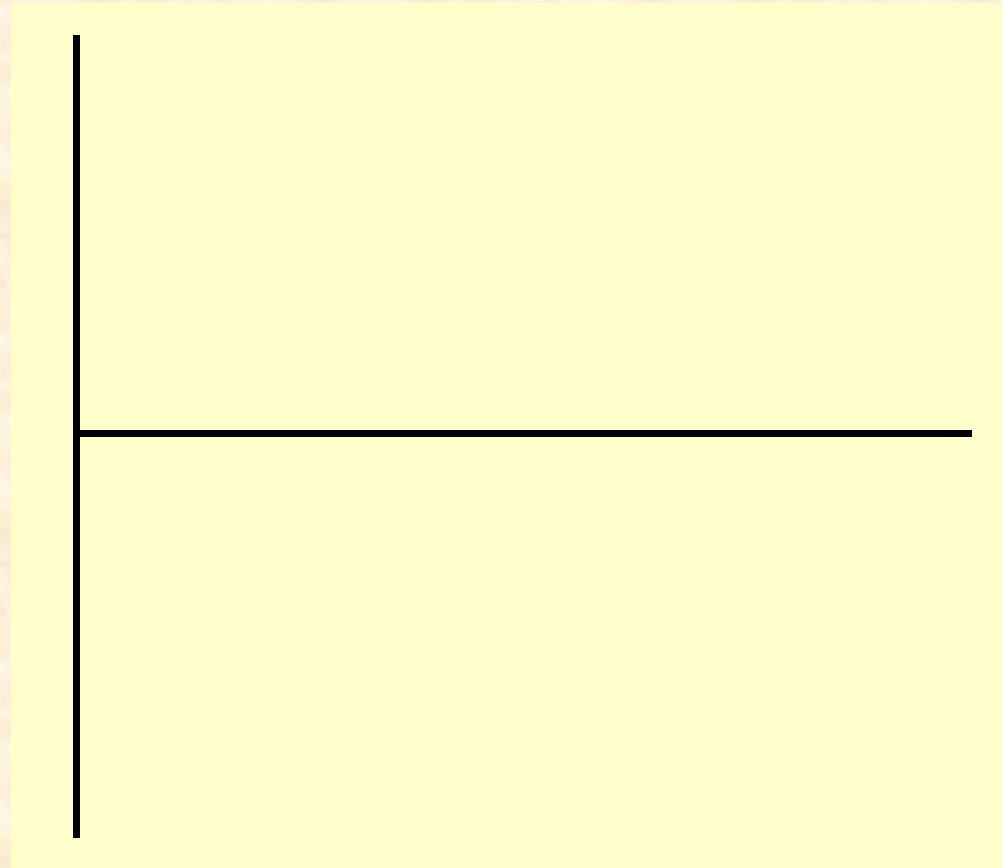
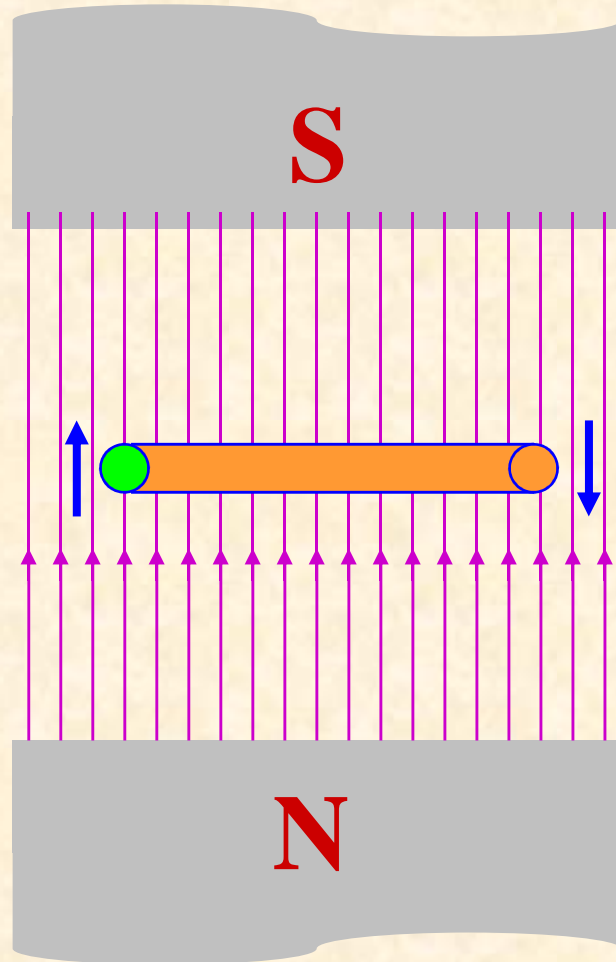


Motion is parallel to the flux

No voltage is induced





Generating Single-Phase Voltage

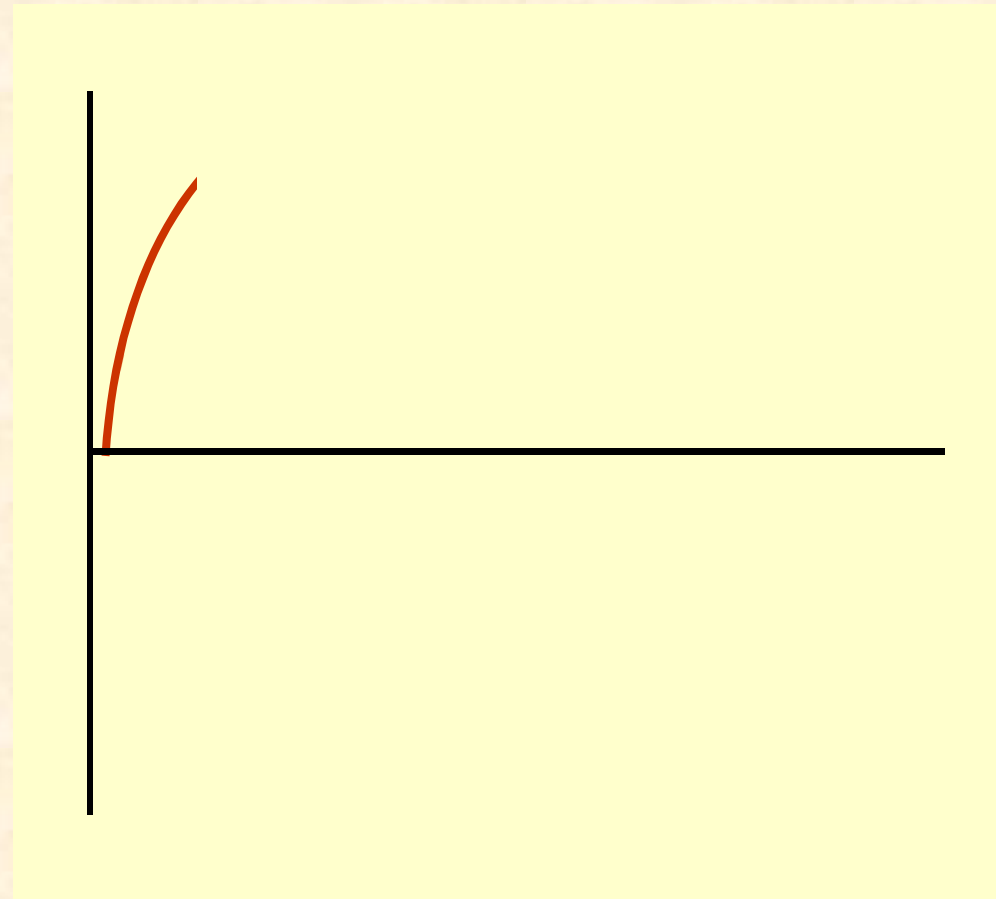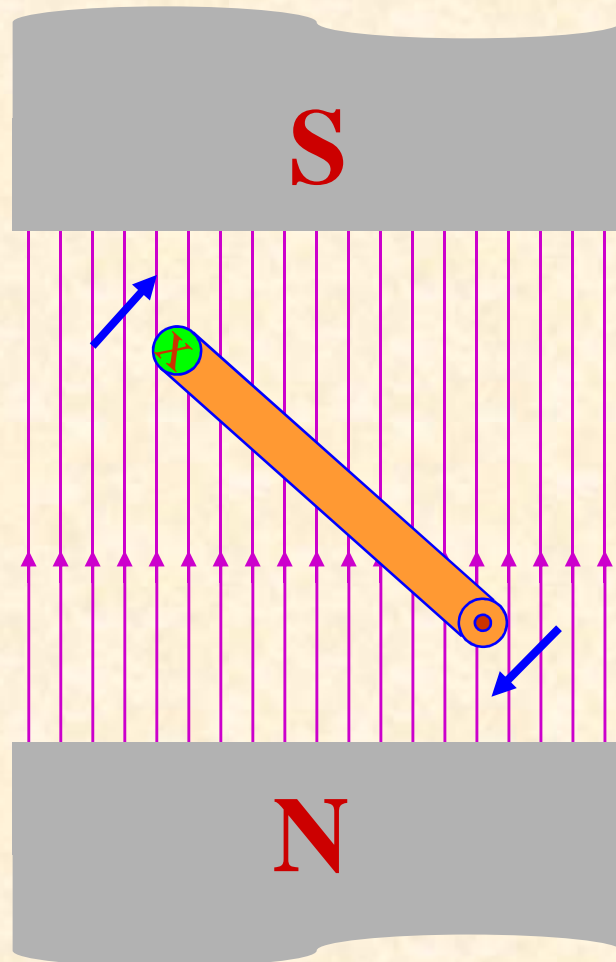

Motion is 45° to flux
Induced voltage is 0.707 of maximum





Generating Single-Phase Voltage

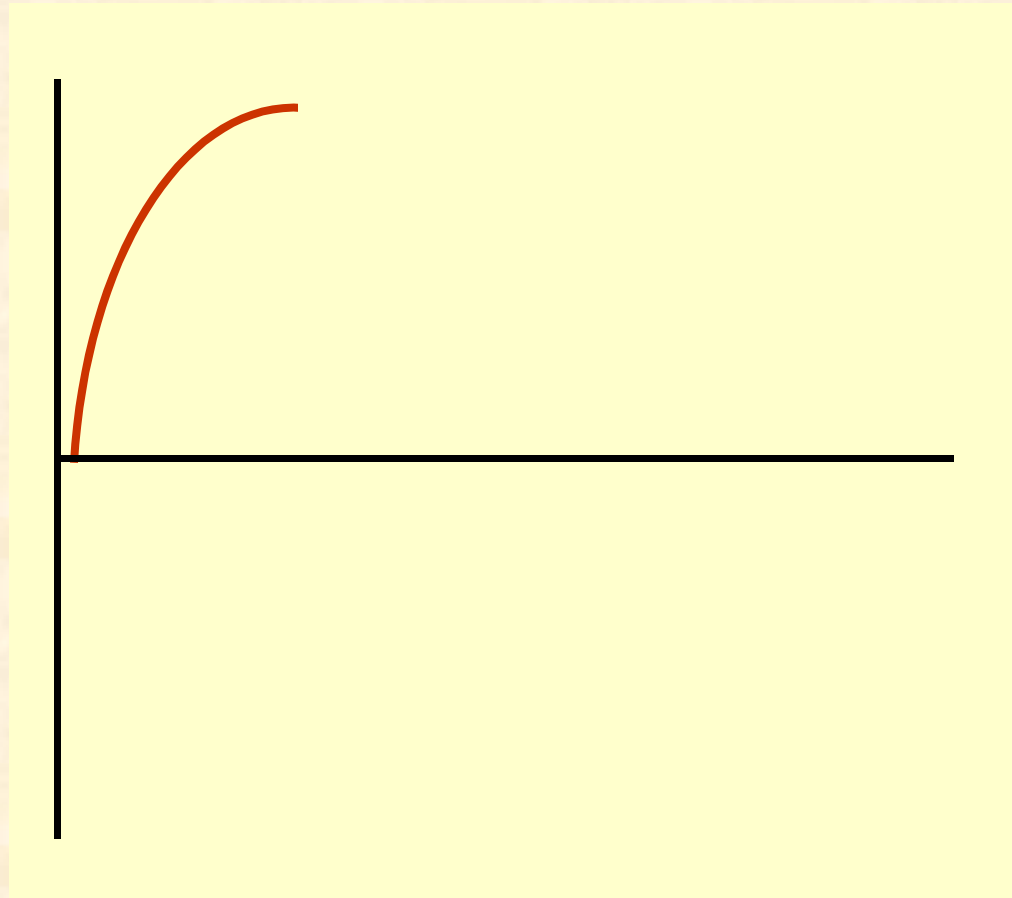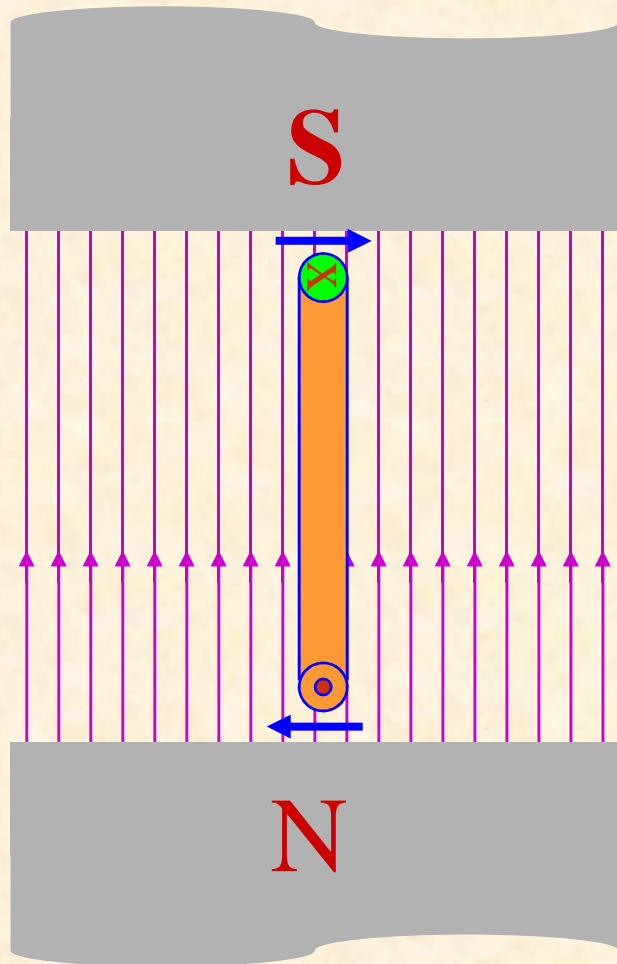

Motion is perpendicular to flux
Induced voltage is maximum





Generating Single-Phase Voltage

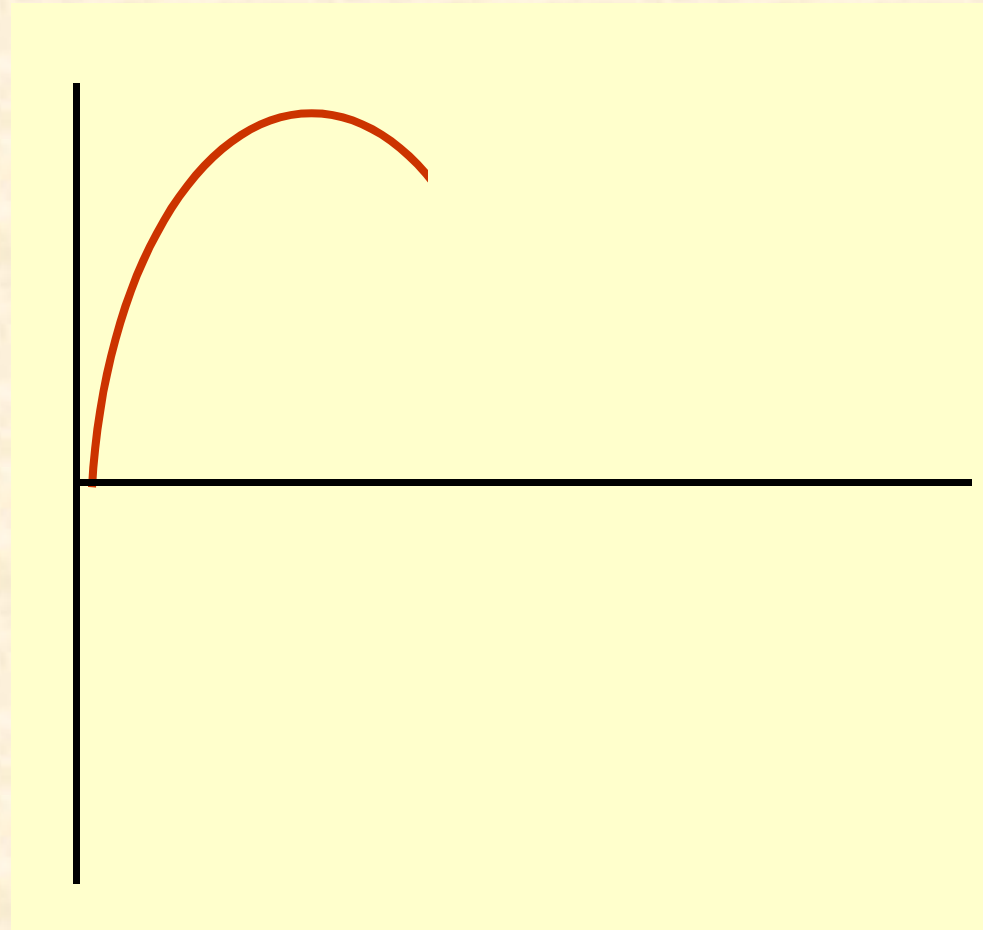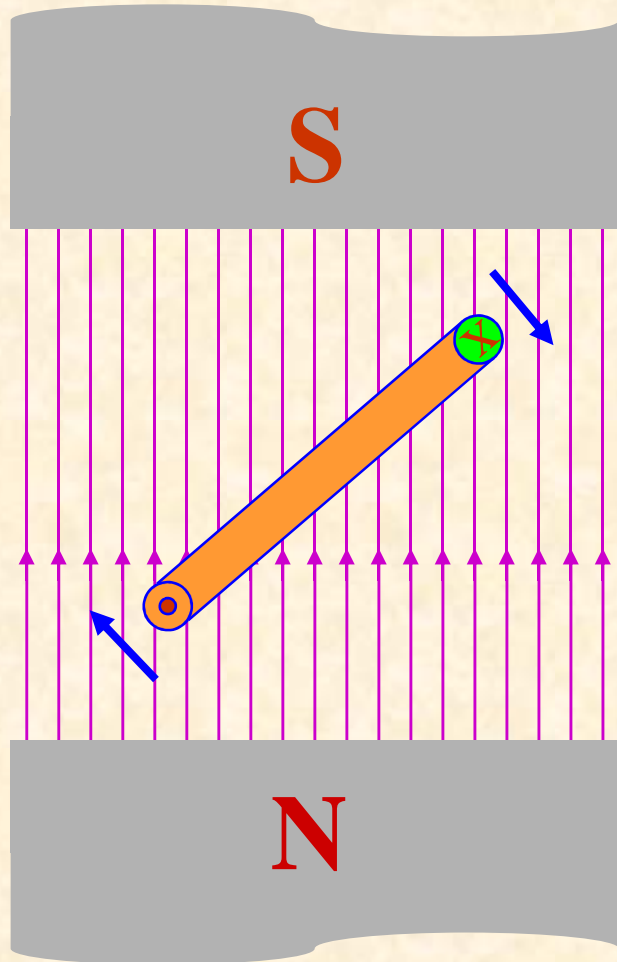

Motion is 45° to flux
Induced voltage is 0.707 of maximum




Generating Single-Phase Voltage

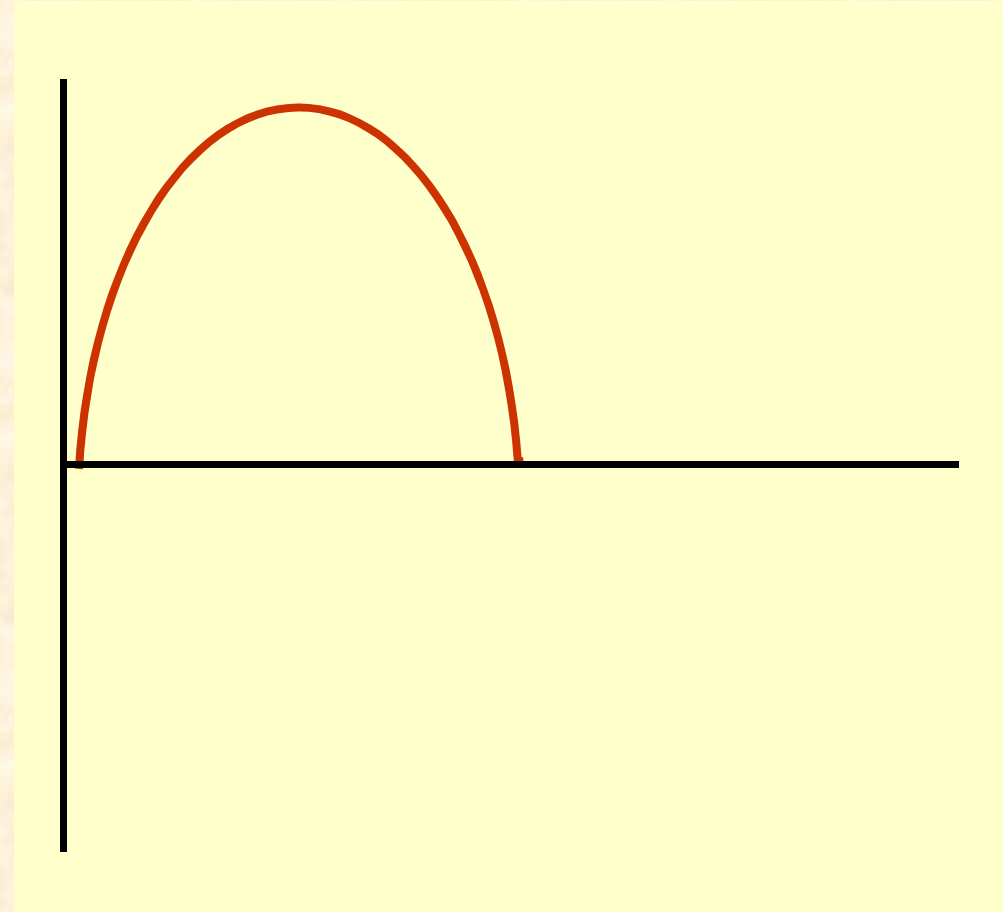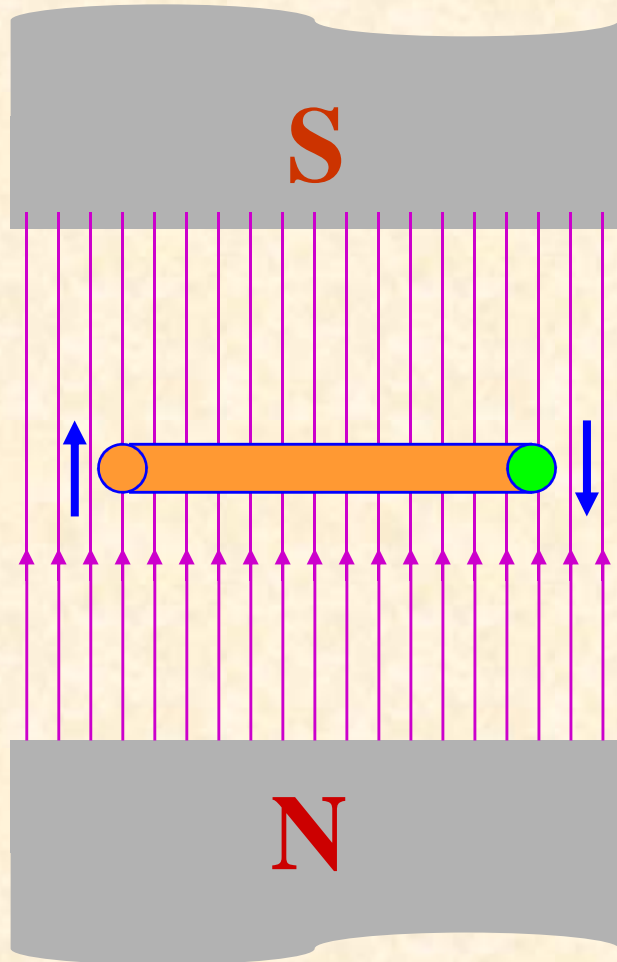


Motion is parallel to flux
No voltage is induced



Generating Single-Phase Voltage

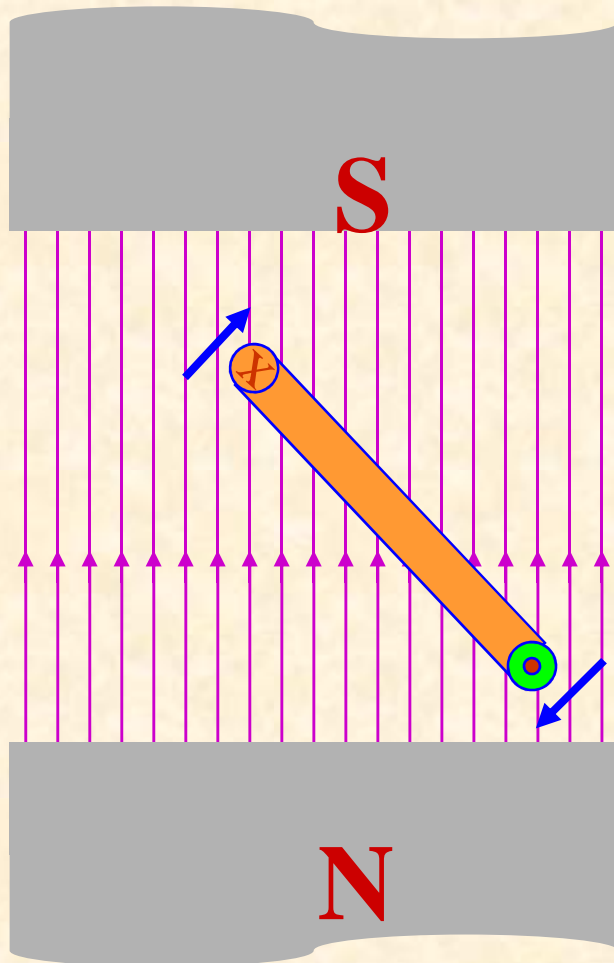


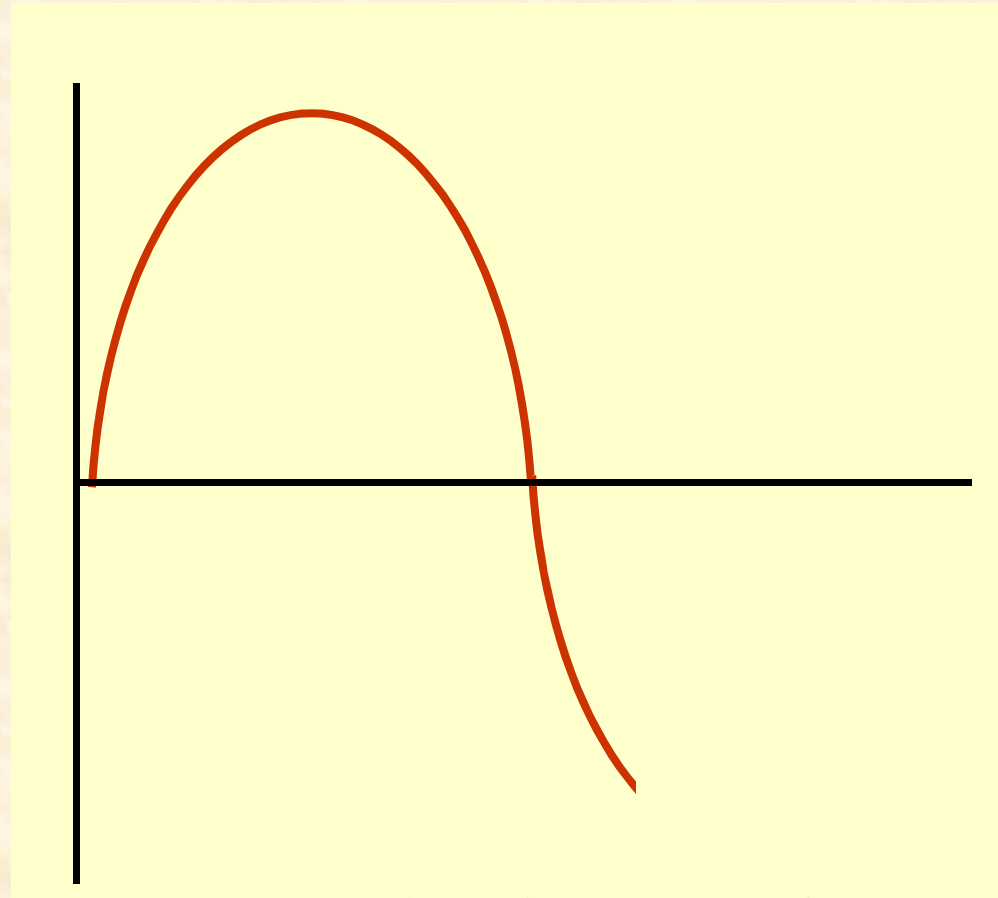
Notice current in the conductor has reversed.



Motion is 45° to flux
Induced voltage is
0.707 of maximum





Generating Single-Phase Voltage

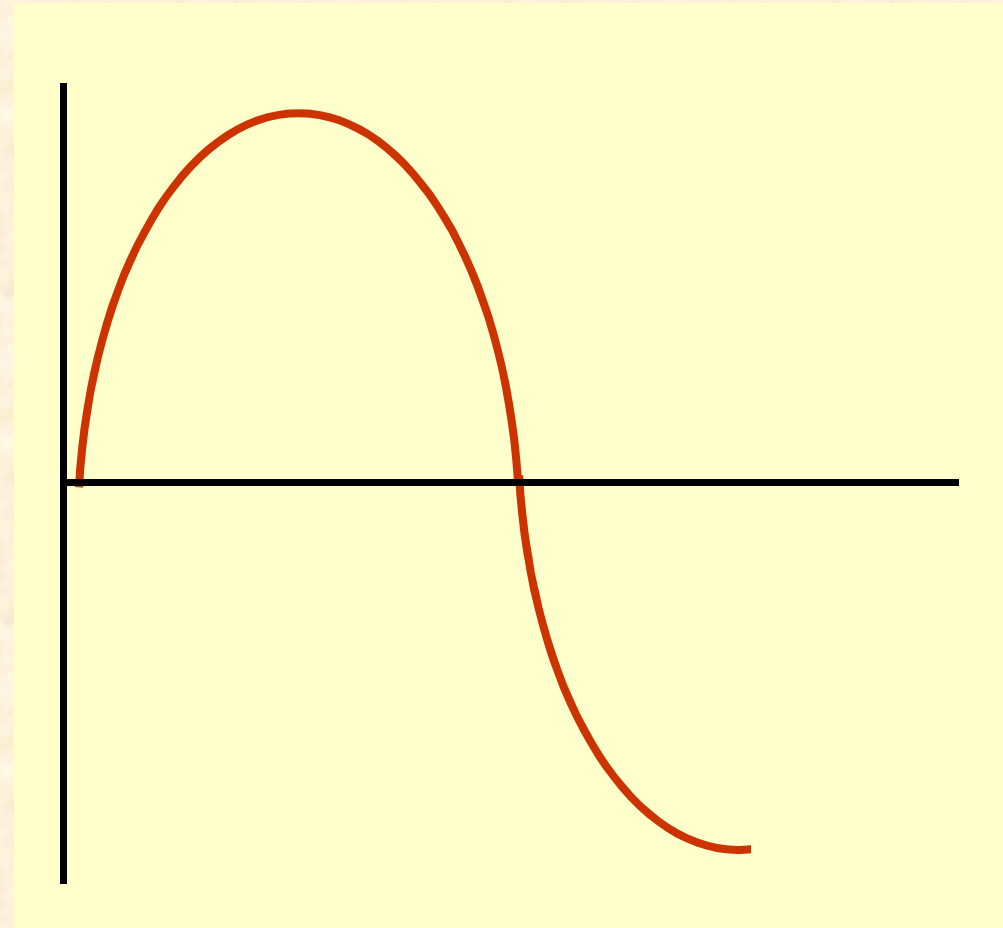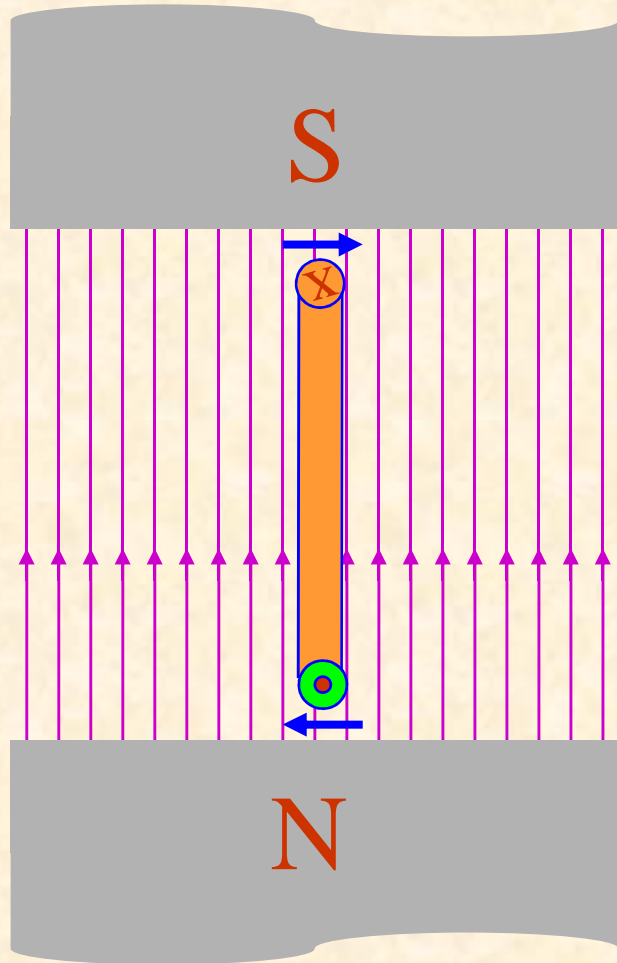

Motion is perpendicular to flux
Induced voltage is maximum



Generating Single-Phase Voltage

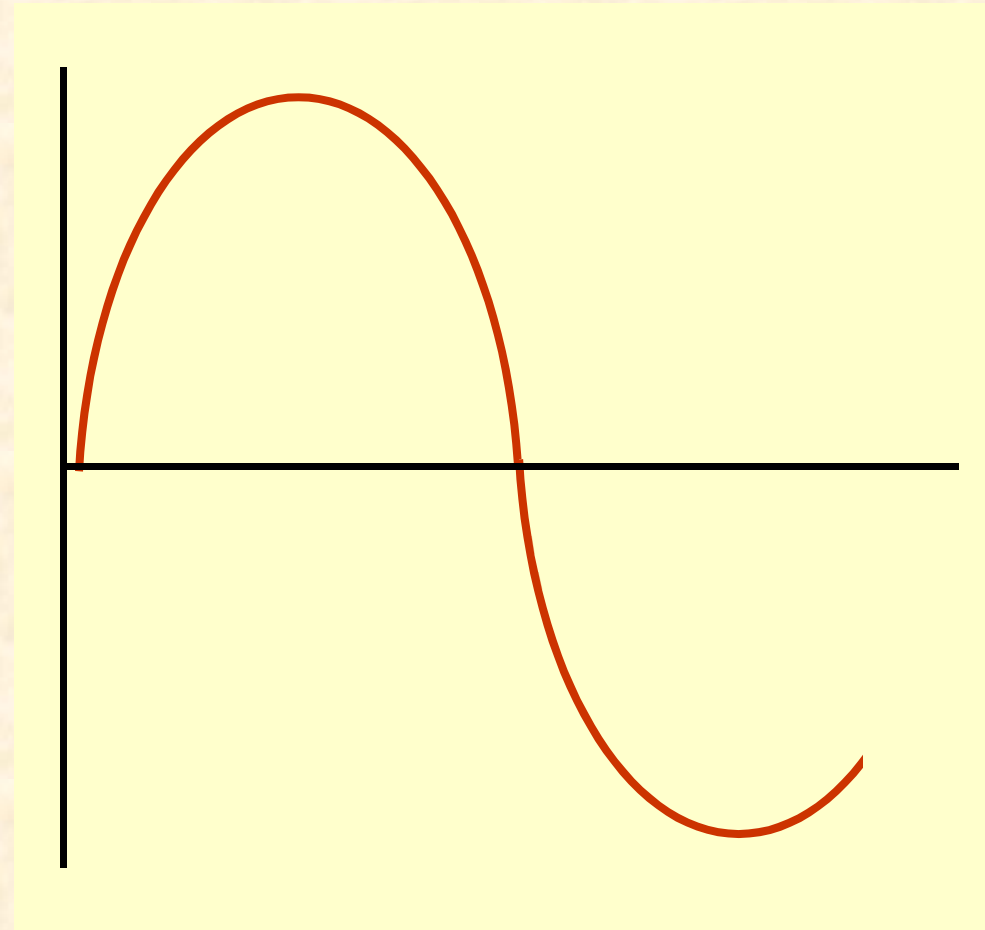
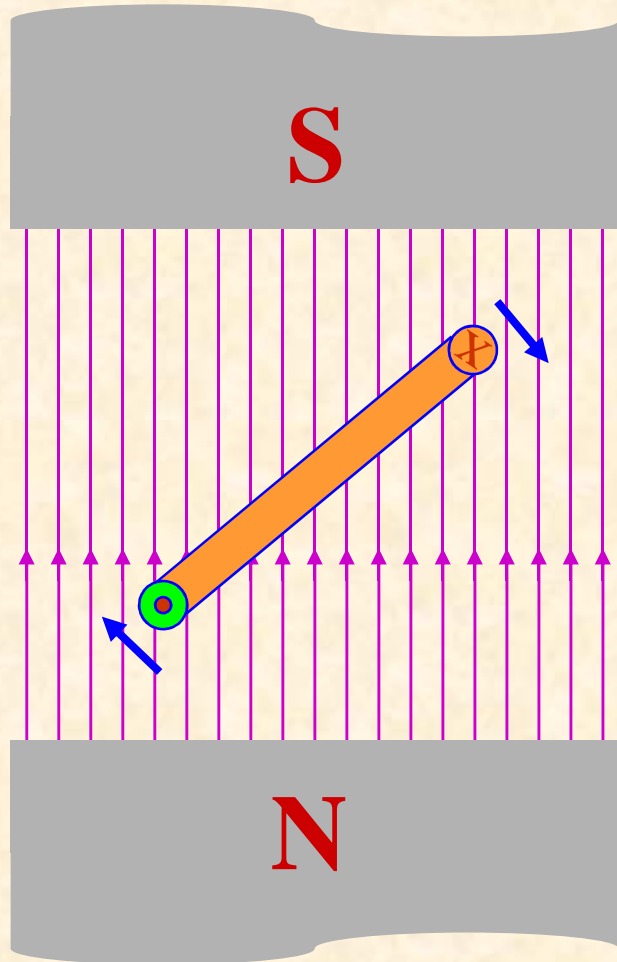


Motion is 45° to flux

Induced voltage is 0.707 of maximum



Generating Single-Phase Voltage

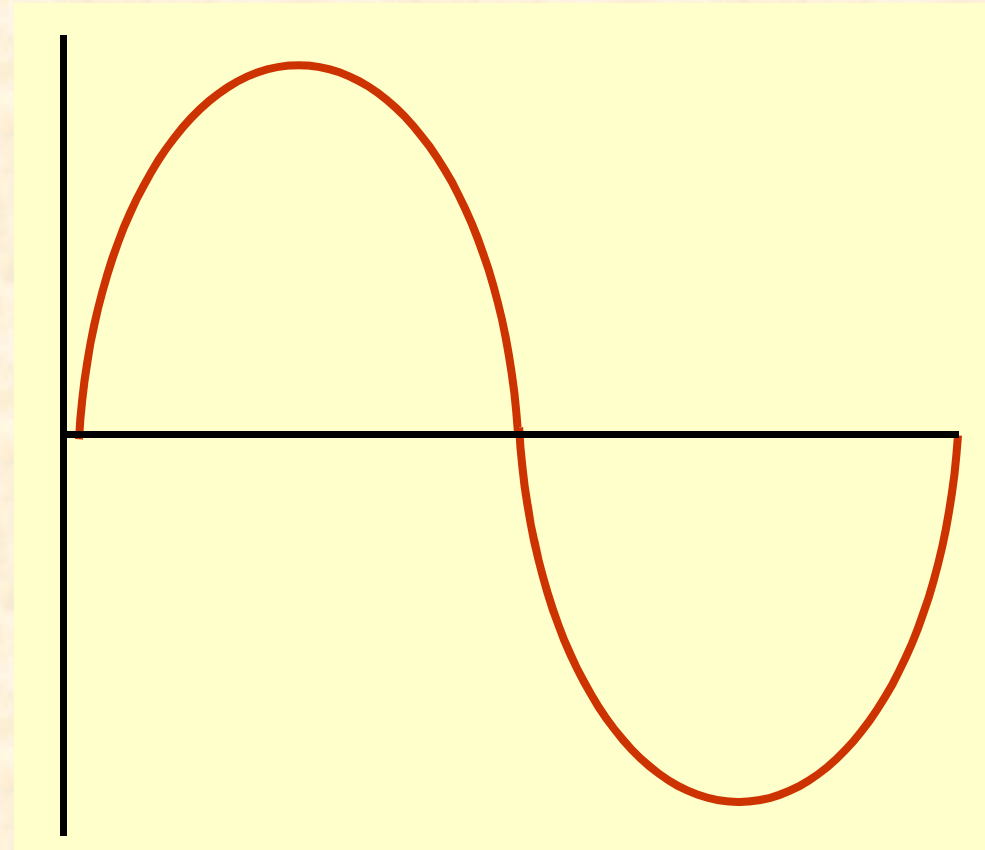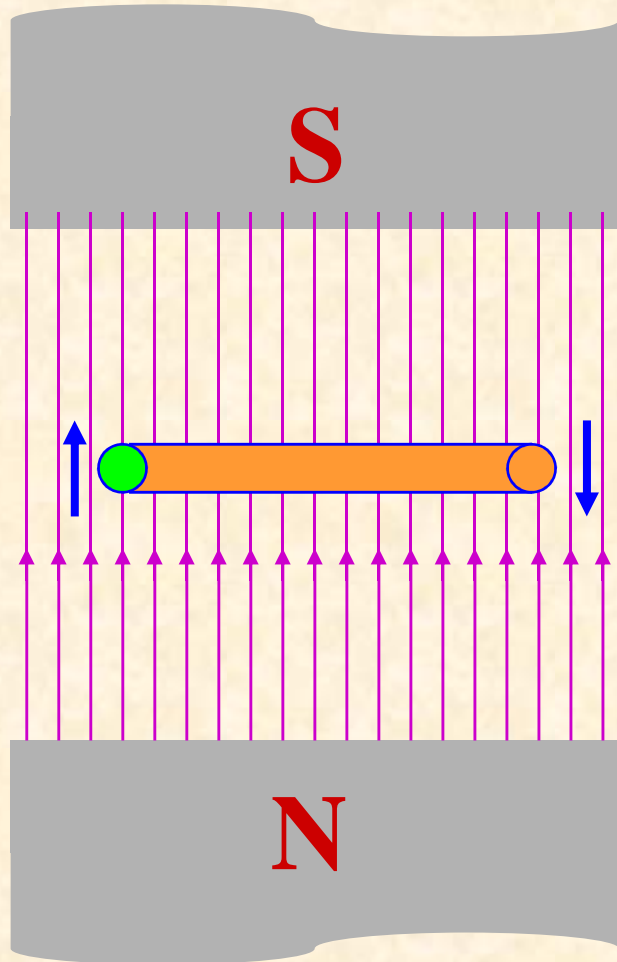

Motion is parallel to flux


No voltage is induced

Ready to produce another cycle




Generating Three-Phase Voltage


Phase-a **Phase-b** **Phase-c**

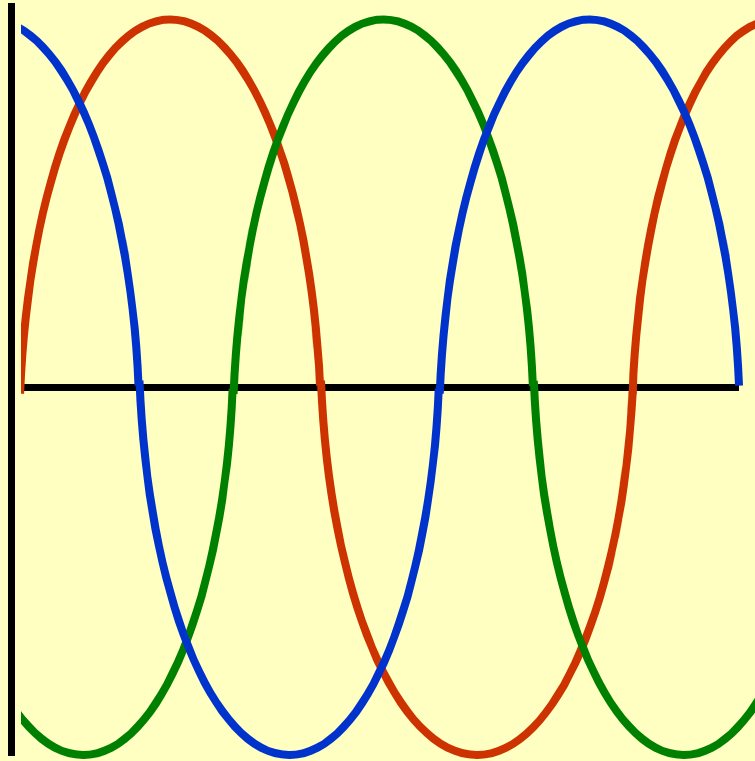

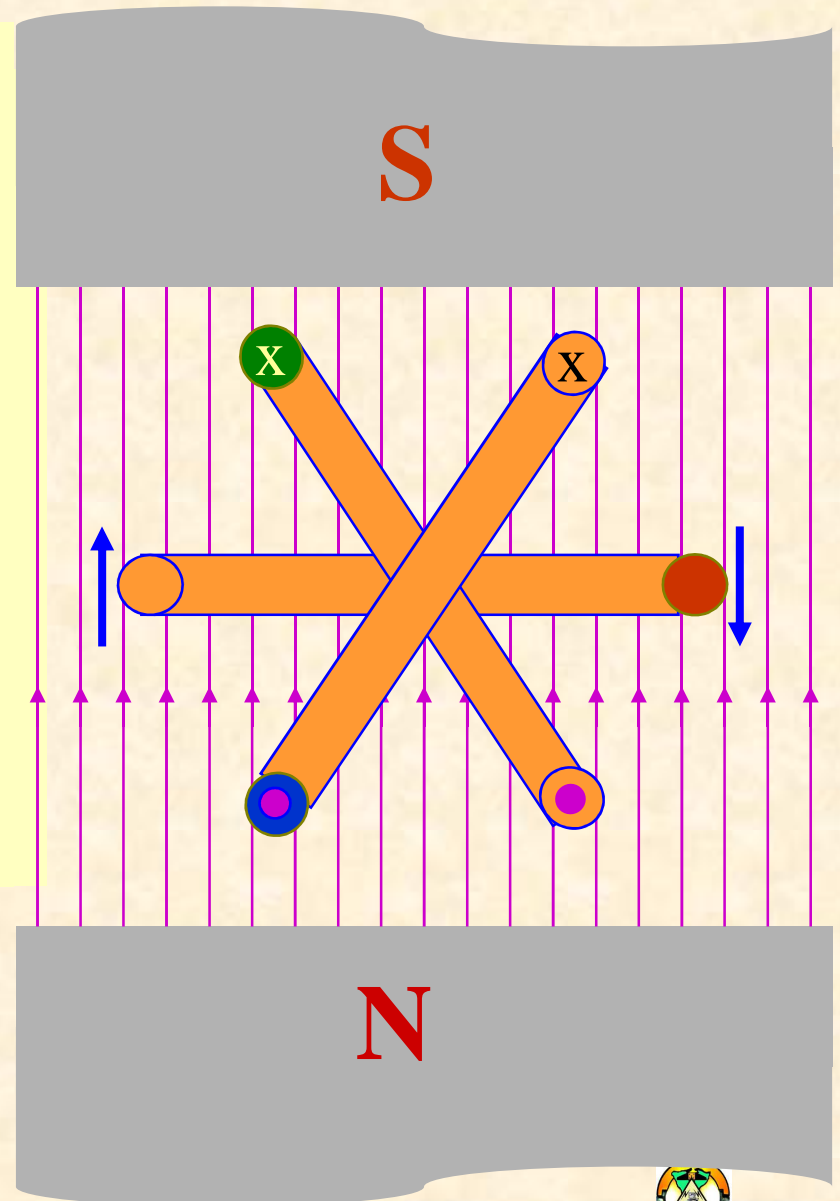Phase-a is ready to go positive
Phase-b is going more negative
Phase-c is going less positive



Generating Three-Phase Voltage

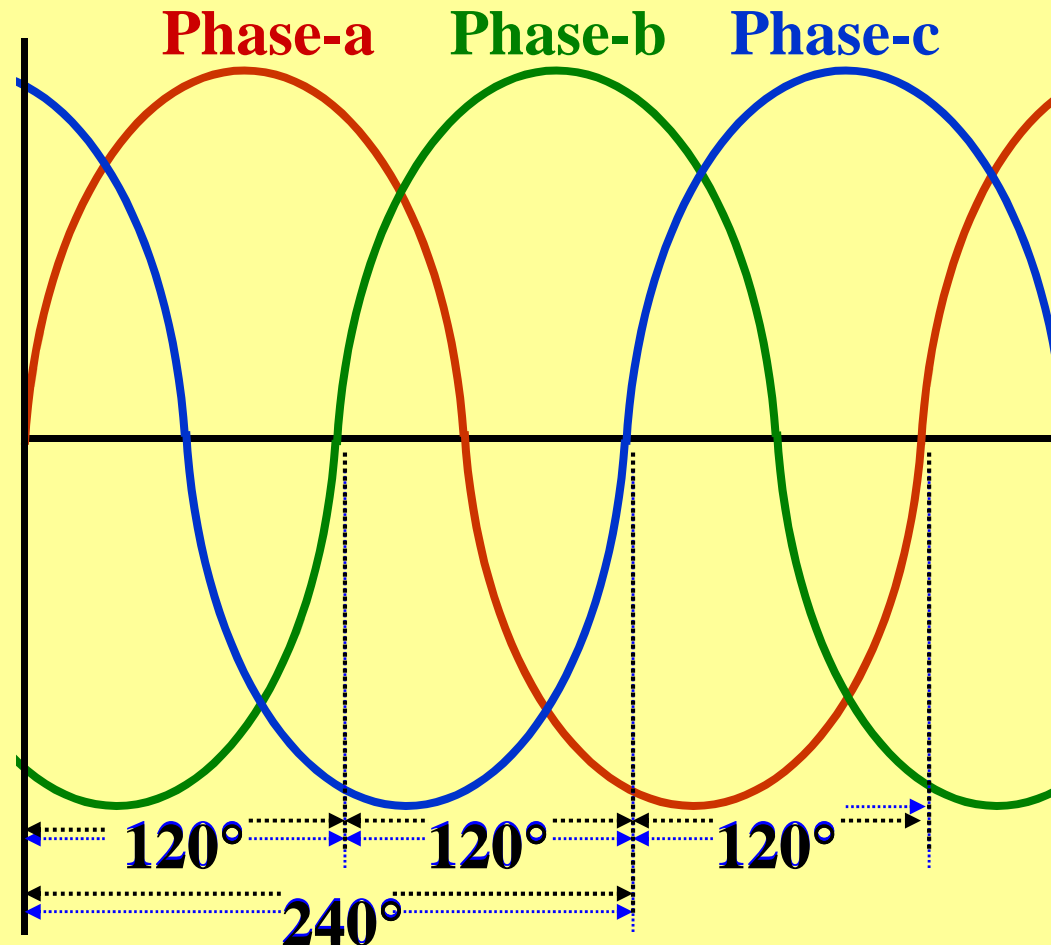

Phase-b lags phase a by 120°
Phase-c lags phase a by 240°

Phase-b leads phase c by 120°
Phase-a leads phase c by 240°



Importance of Three-Phase System

- ❑ All electric power is generated and distributed in three phase
- ✓ One phase, two phase, can be taken from three phase system rather than generated independently
- ✓ The instantaneous power in a 3ϕ system can be constant (not pulsating)
- ✓ High power motors prefer a steady torque especially one created by a rotating magnetic field
- ✓ Three phase system is more economical than the single phase
- ✓ The amount of wire required for a three phase system is less than required for an equivalent single phase system




Three-Phase Generator

- The generator consists of a rotating magnet (**rotor**) surrounded by a stationary winding (**stator**)
- Three separate windings or coils with terminals a-a', b-b', and c-c' are physically placed 120° apart around the stator
- As the rotor rotates, its magnetic field cuts the flux from the three coils and induces voltages in the coils
- The induced voltage have equal magnitude but out of phase by 120°




Three-Phase Generator

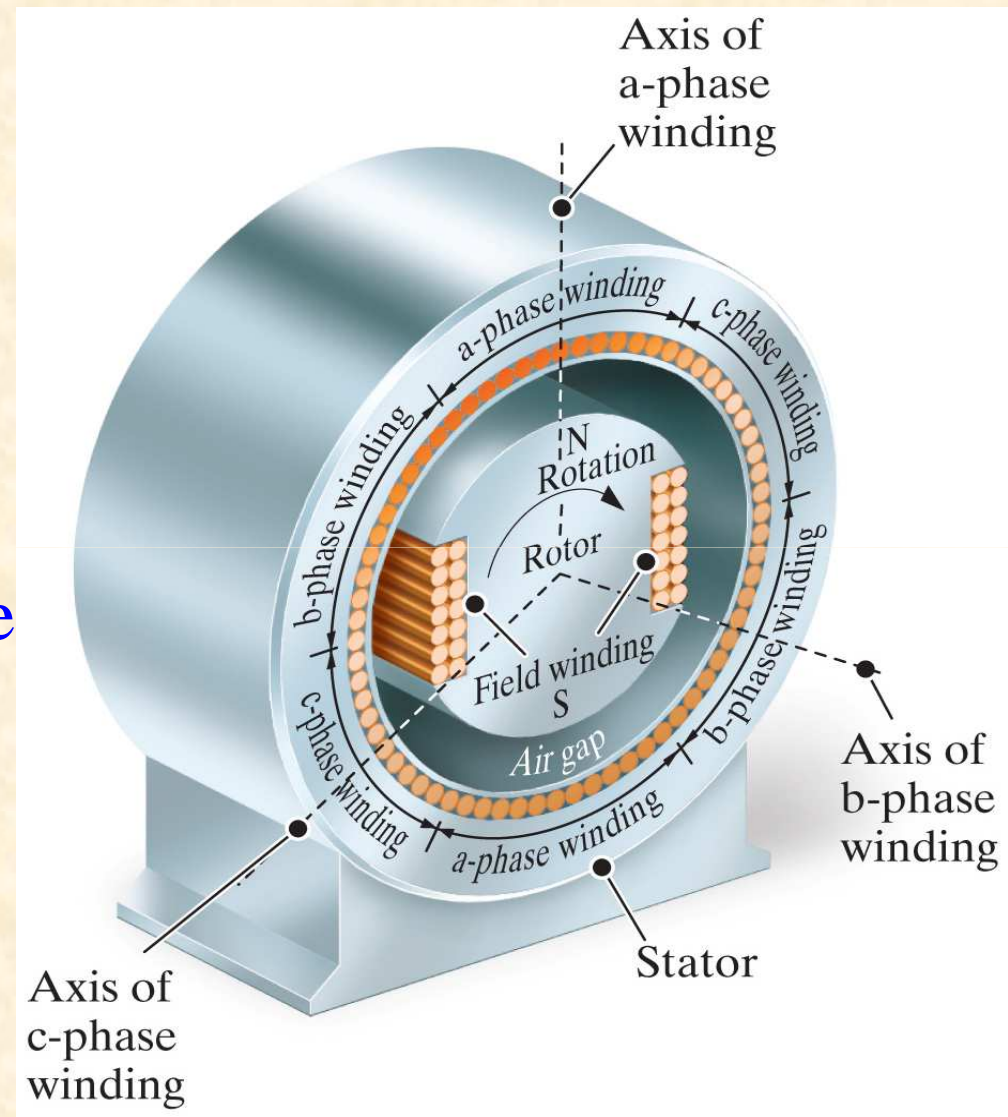
- ✓ 2-pole (North-South) rotor turned by a “prime mover”
- ✓ Sinusoidal voltages are induced in each stator winding




Three-Phase Generator

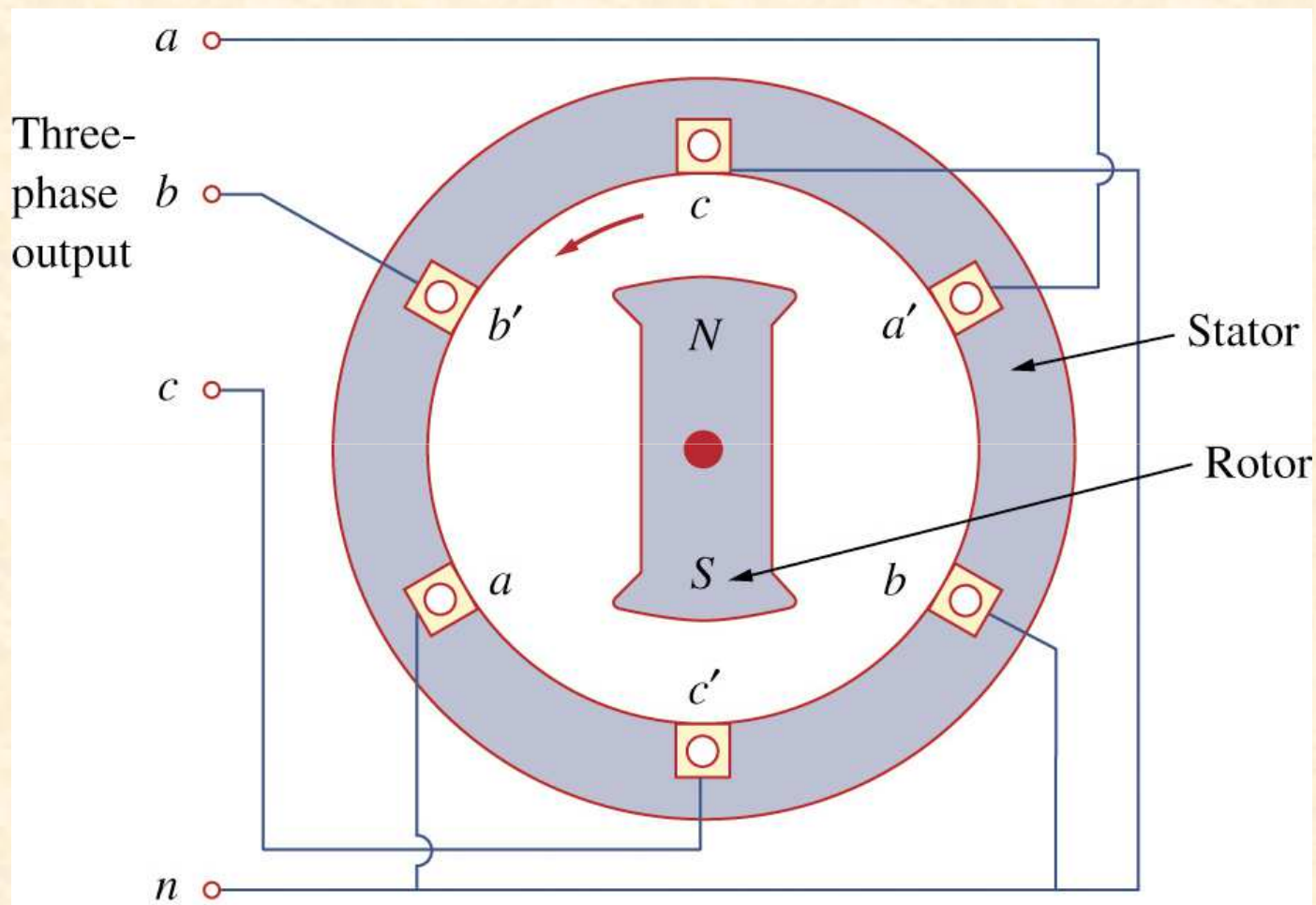


Three-Phase Voltages

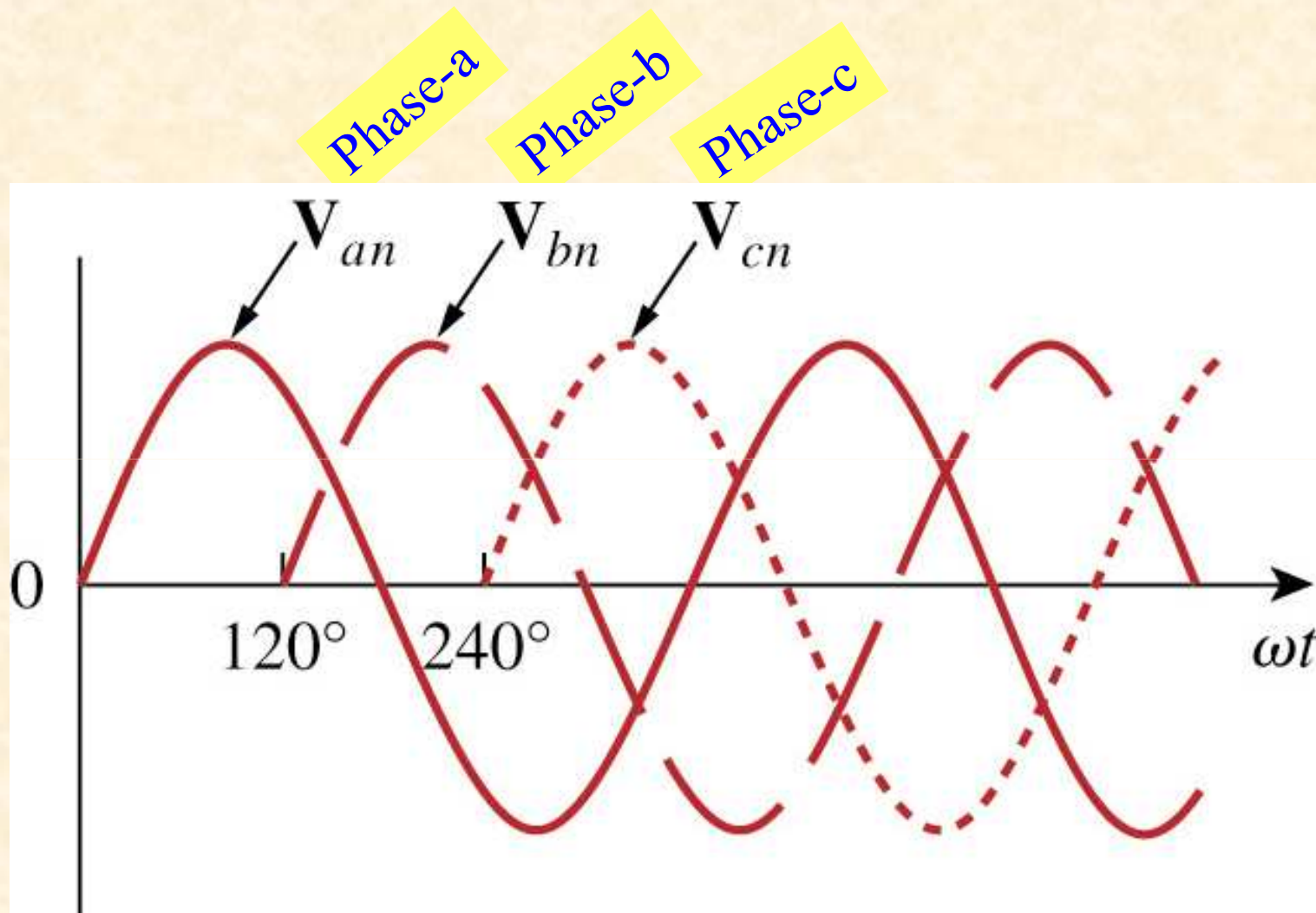

Basic Three-Phase Circuit

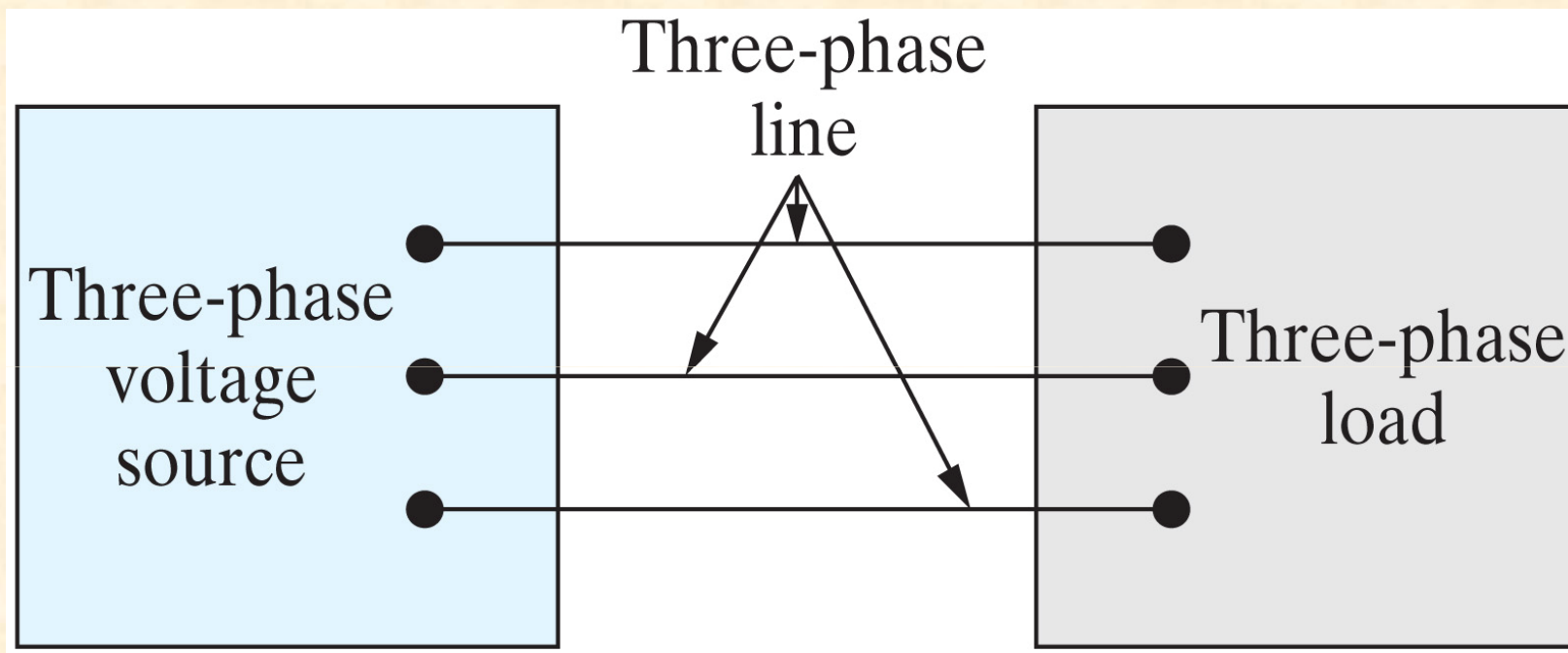

Three-Phase Voltages Sources

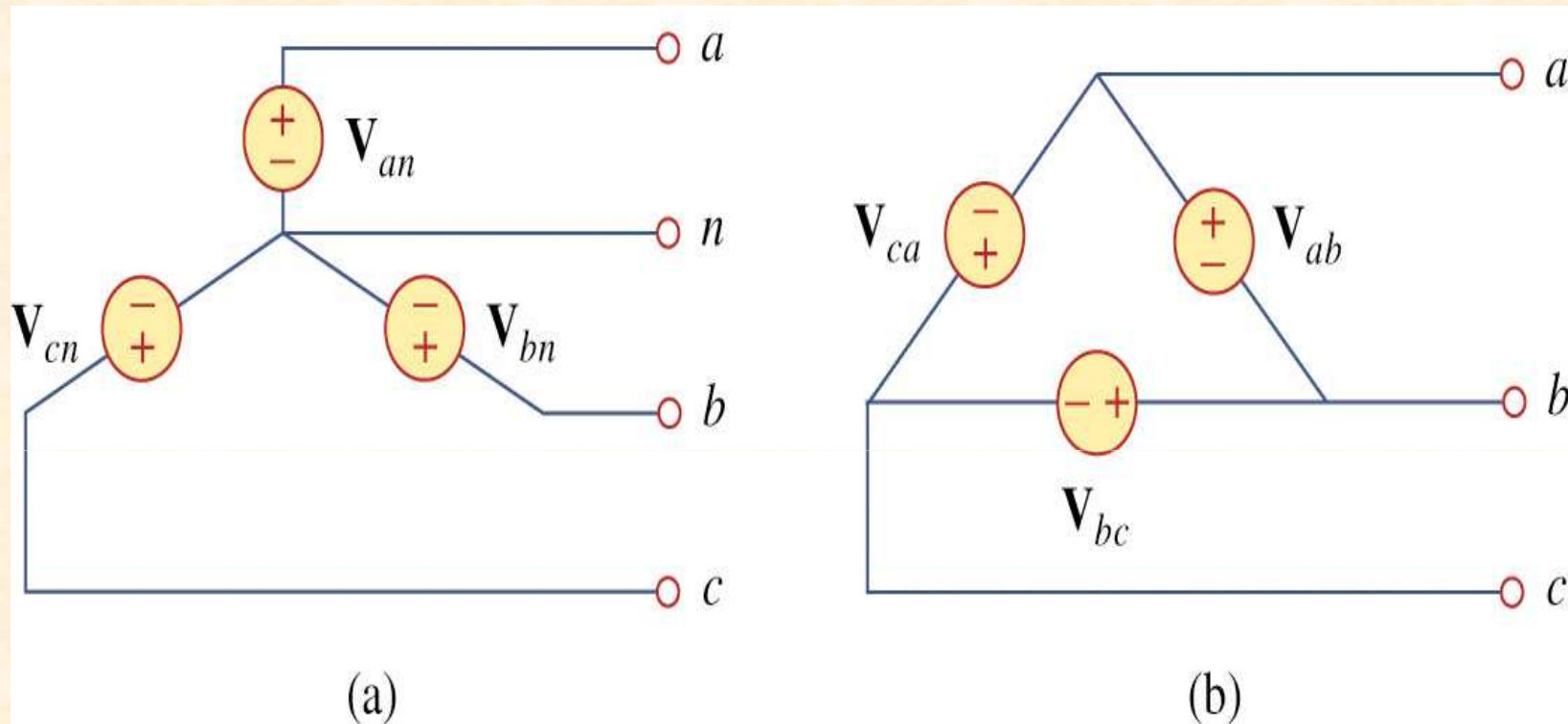


Y-connected Source

Δ -connected Source




Balanced Three-Phase Voltages Sources

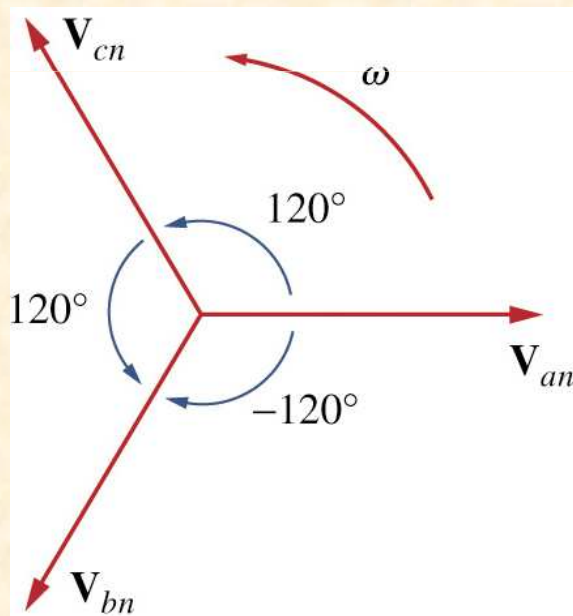- Balanced phase voltages are equal in magnitude and are out of phase with one another by 120 degrees
- Phase voltages sum up to zero ($V_{an} + V_{bn} + V_{cn} = 0$)
- There are two possible combinations:



abc or (+) sequence

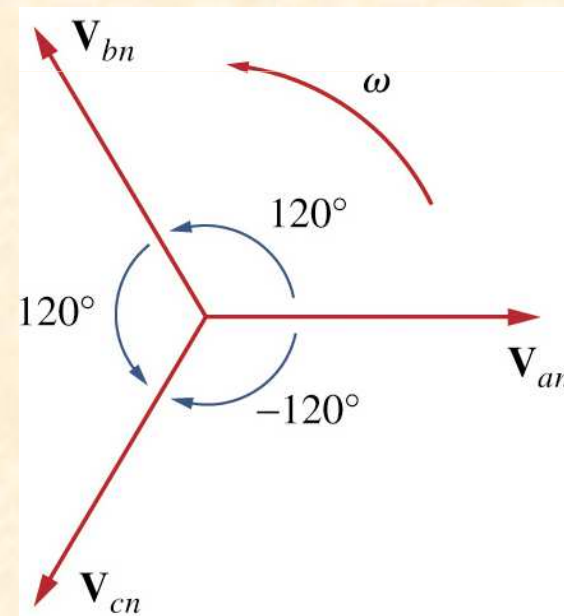

acb or (-) sequence



Balanced Three-Phase Voltages

$$v_{an}(t) = V_M \cos(\omega t)$$

$$v_{bn}(t) = V_M \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_M \cos(\omega t - 240^\circ) = V_M \cos(\omega t + 120^\circ)$$

$$V_{an} = V_M \angle 0^\circ$$

$$V_{bn} = V_M \angle -120^\circ$$

$$V_{cn} = V_M \angle +120^\circ$$

POSITIVE SEQUENCE

$$V_{an} = V_M \angle 0^\circ$$

$$V_{bn} = V_M \angle +120^\circ$$


$$V_{cn} = V_M \angle -120^\circ$$

NEGATIVE SEQUENCE




Balanced Three-Phase Load Configurations

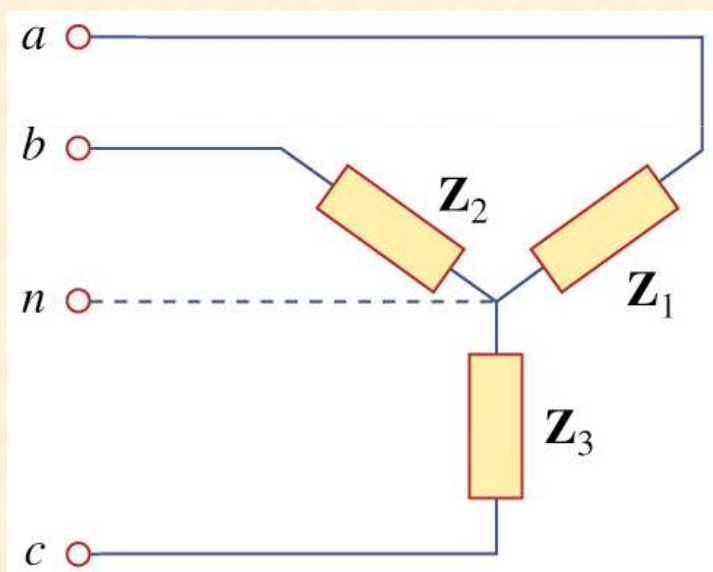- A balanced three-phase load is one in which the phase impedances are equal in magnitude and in phase



Y-connected Load

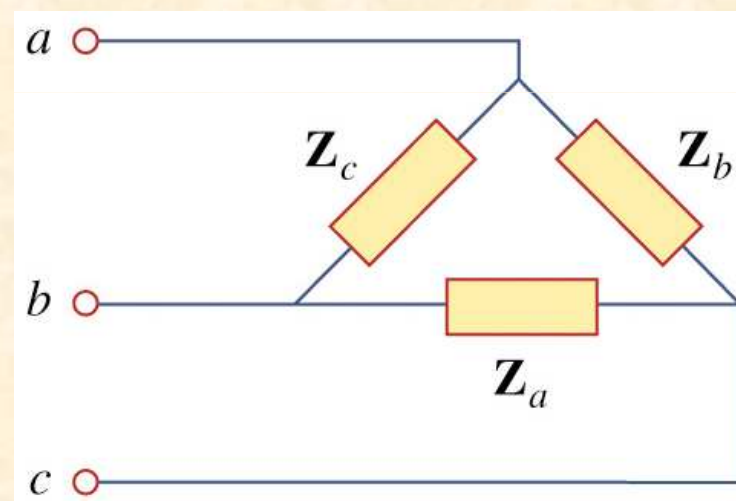

Δ-connected Load



Source-Load Connection

SOURCE	LOAD	CONNECTION
Wye	Wye	Y-Y
Wye	Delta	Y- Δ
Delta	Delta	Δ - Δ
Delta	Wye	Δ -Y



Three-Phase Quantities

QUANTITY	SYMBOL
Phase current	I_{ϕ}
Line current	I_L
Phase voltage	V_{ϕ}
Line voltage	V_L



Phase Voltages and Line Voltages & Currents

- ❑ Phase voltage, (V_ϕ) is measured between the neutral and any line: line to neutral voltage
- ❑ Line voltage, (V_L) is measured between any two of the three lines: line to line voltage
- ❑ Line current, (I_L) is the current in each line of the source or load
- ❑ Phase current, (I_ϕ) is the current in each phase of the source or load



Balanced Y- Connected Voltage Source

✓ Line currents equal phase Currents


$$I_L = I_\phi$$

✓ Phase voltages are

(V_{an}, V_{bn}, V_{cn})

✓ Line voltages are

(V_{ab}, V_{bc}, V_{ca})

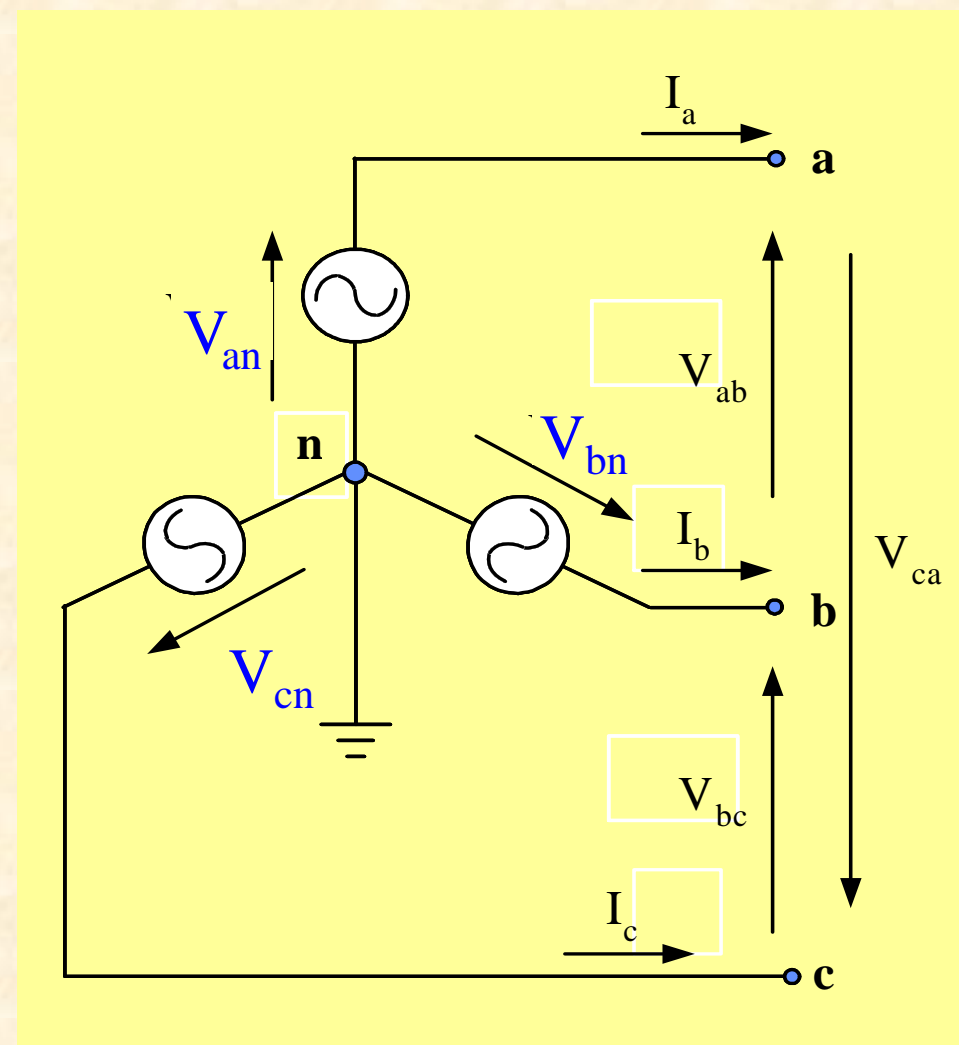

Phase Diagram of Line and Phase Voltages (+ve Sequence)

□ PHASE VOLTAGE

$$V_{an} = V_M \angle 0^\circ \quad \text{volt}$$

$$V_{bn} = V_M \angle -120^\circ \quad \text{volt}$$


$$V_{cn} = V_M \angle 120^\circ \quad \text{volt}$$

□ LINE VOLTAGE

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

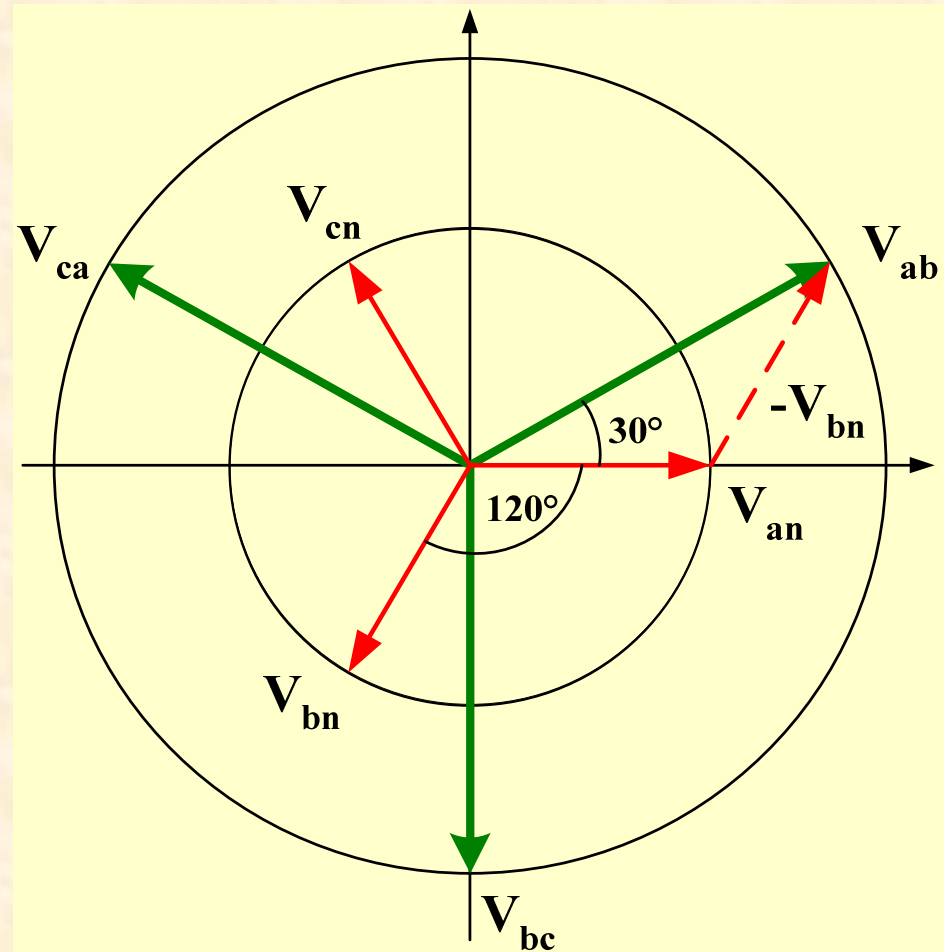

Relation Between Line and Phase Voltages (+ve Sequence)

**LINE
VOLTAGE
(V_L)**

$$\left\{ \begin{array}{l} V_{ab} = \sqrt{3} V_M \angle 30^\circ \text{ volt} \\ V_{bc} = \sqrt{3} V_M \angle -90^\circ \text{ volt} \\ V_{ca} = \sqrt{3} V_M \angle 150^\circ \text{ volt} \end{array} \right.$$



$$|V_L| = \sqrt{3} |V_\phi|$$

$$\angle V_L = \angle V_\phi + 30^\circ$$




Conclusions for Balanced Y-connected Voltage Source

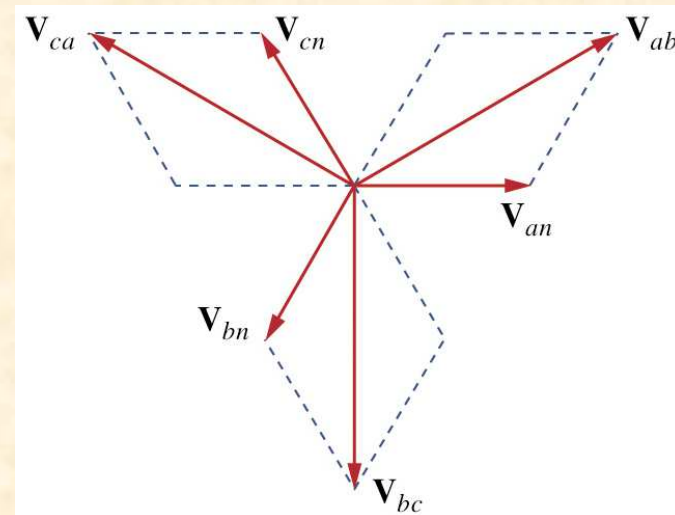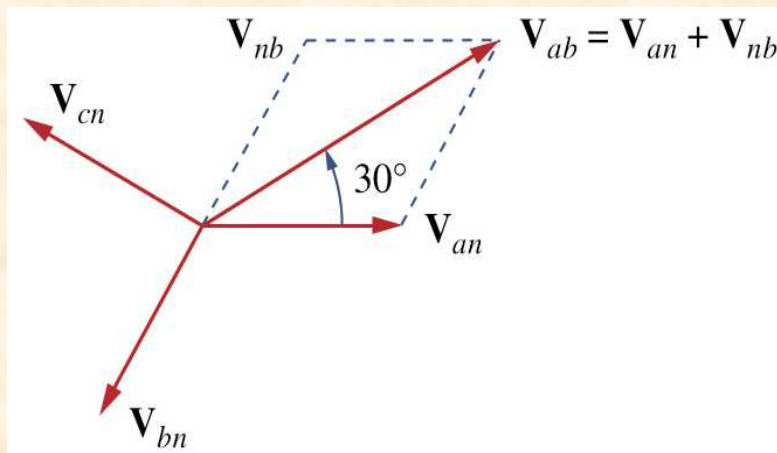
- Balanced line voltages are equal in magnitude and are out of phase with one another by 120 degrees
- Line voltages sum up to zero ($V_{ab} + V_{bc} + V_{ca} = 0$)
- The magnitude of line voltages is $\sqrt{3}$ times the magnitude of the phase voltages
- Line Voltages lead their corresponding phase voltages by 30 degrees (for +ve sequence)



Balanced Y-connected Load

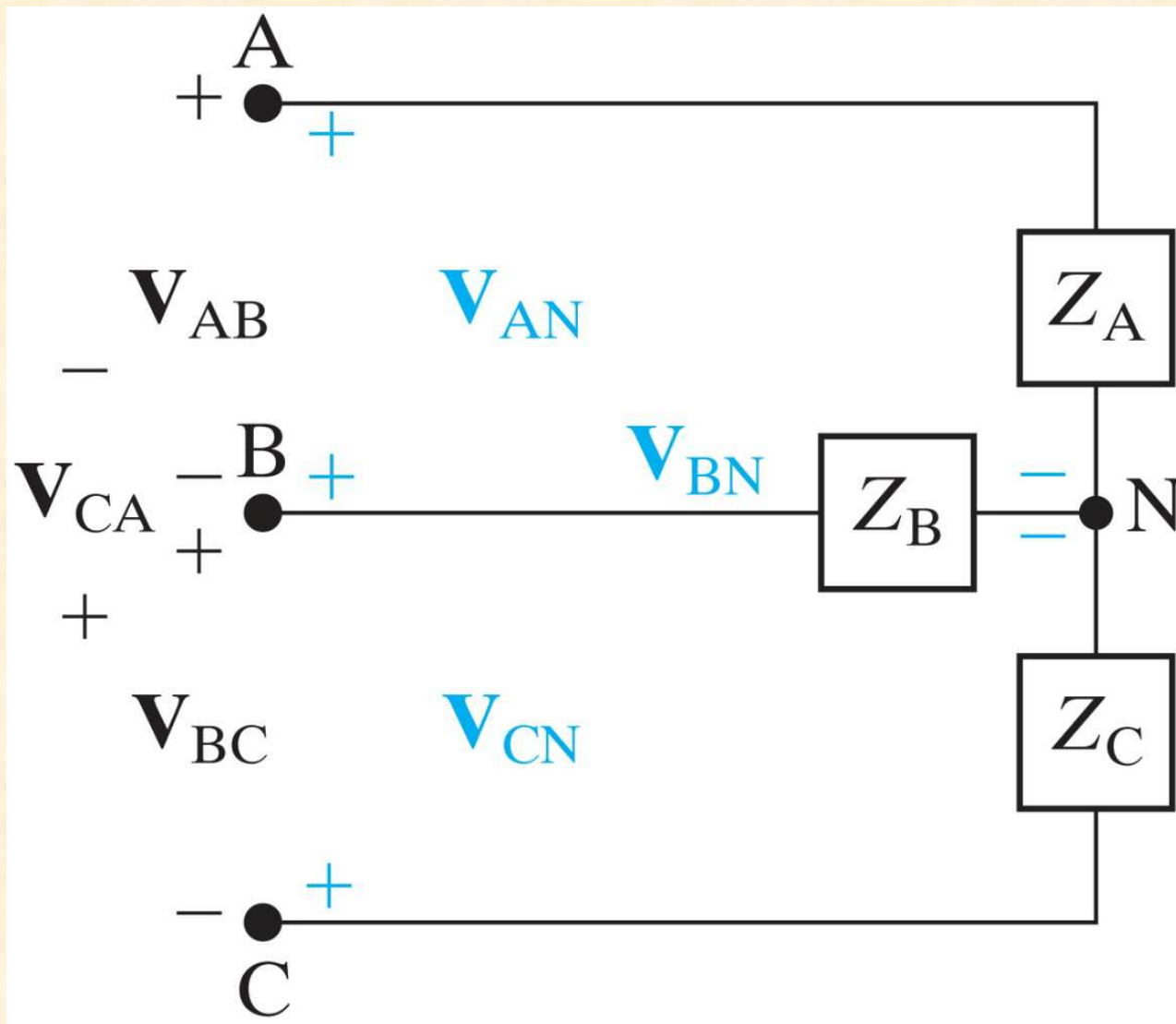

Balanced Y-connected Load

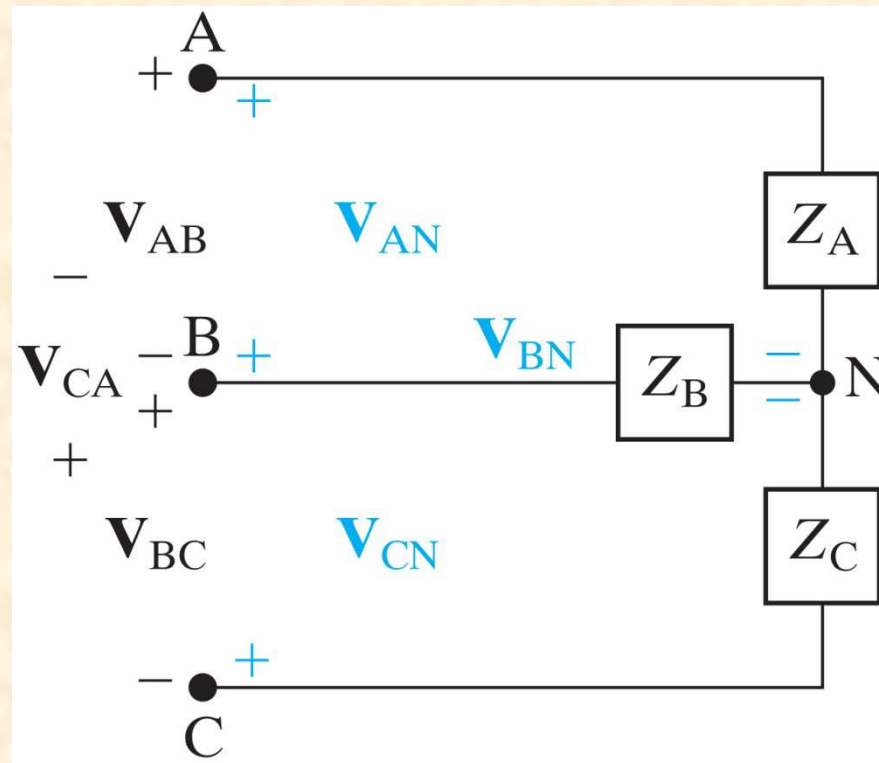

Line Voltages

$$V_{AB} = V_{AN} - V_{BN}$$


$$V_{BC} = V_{BN} - V_{CN}$$

$$V_{CA} = V_{CN} - V_{AN}$$

Phase Voltages



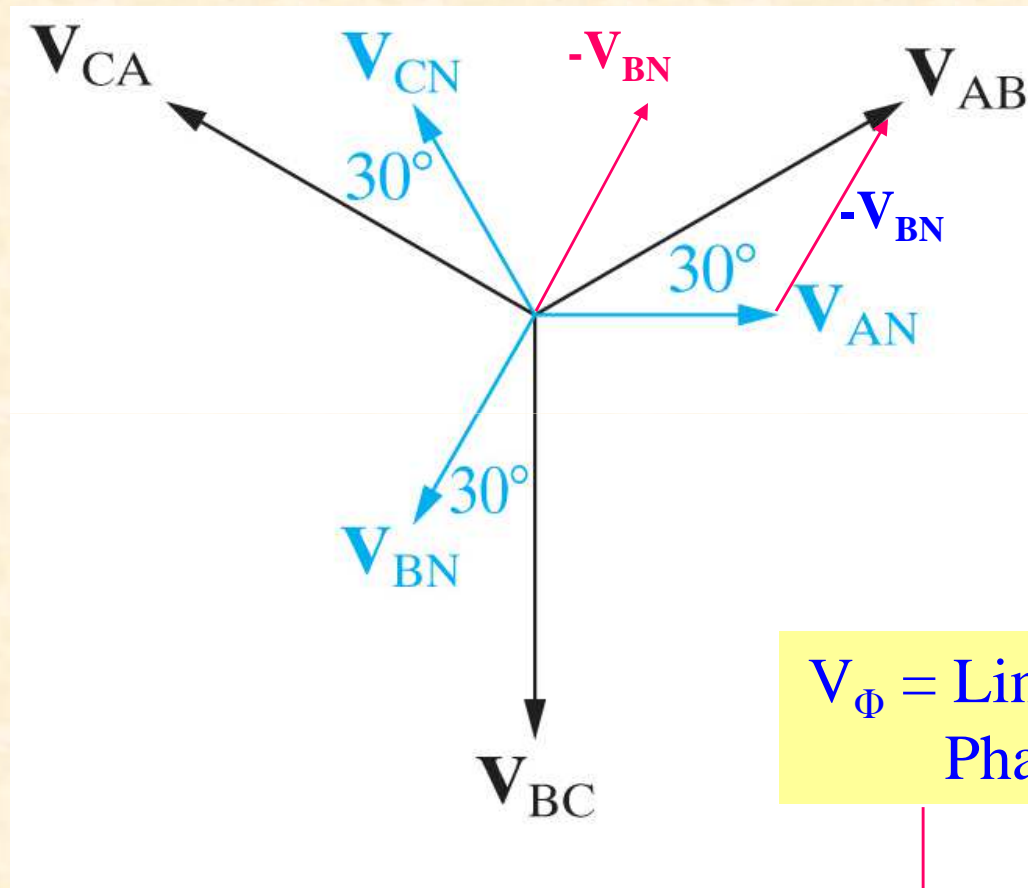Line and Phase Voltages for Balanced Y-connected Load



V_{Φ} = Line-to-Neutral, or
Phase Voltage

$$V_{AB} = V_{AN} - V_{BN} = \sqrt{3} V_{\Phi}$$




Conclusions for Balanced Y-Connected System

- The Line currents equal phase Currents
- The amplitude of the line-to-line voltage is equal to $\sqrt{3}$ times the amplitude of the phase voltage
- The line-to-line voltages form a balanced set of 3-phase voltages
- The set of line-to-line voltages leads the set of line-to-neutral (phase) voltages by 30° (for +ve sequence)
- The set of line-to-line voltages lags the set of line-to-neutral (phase) voltages by 30° (for -ve sequence)



Y-Y Three-Phase System (Four Wire)

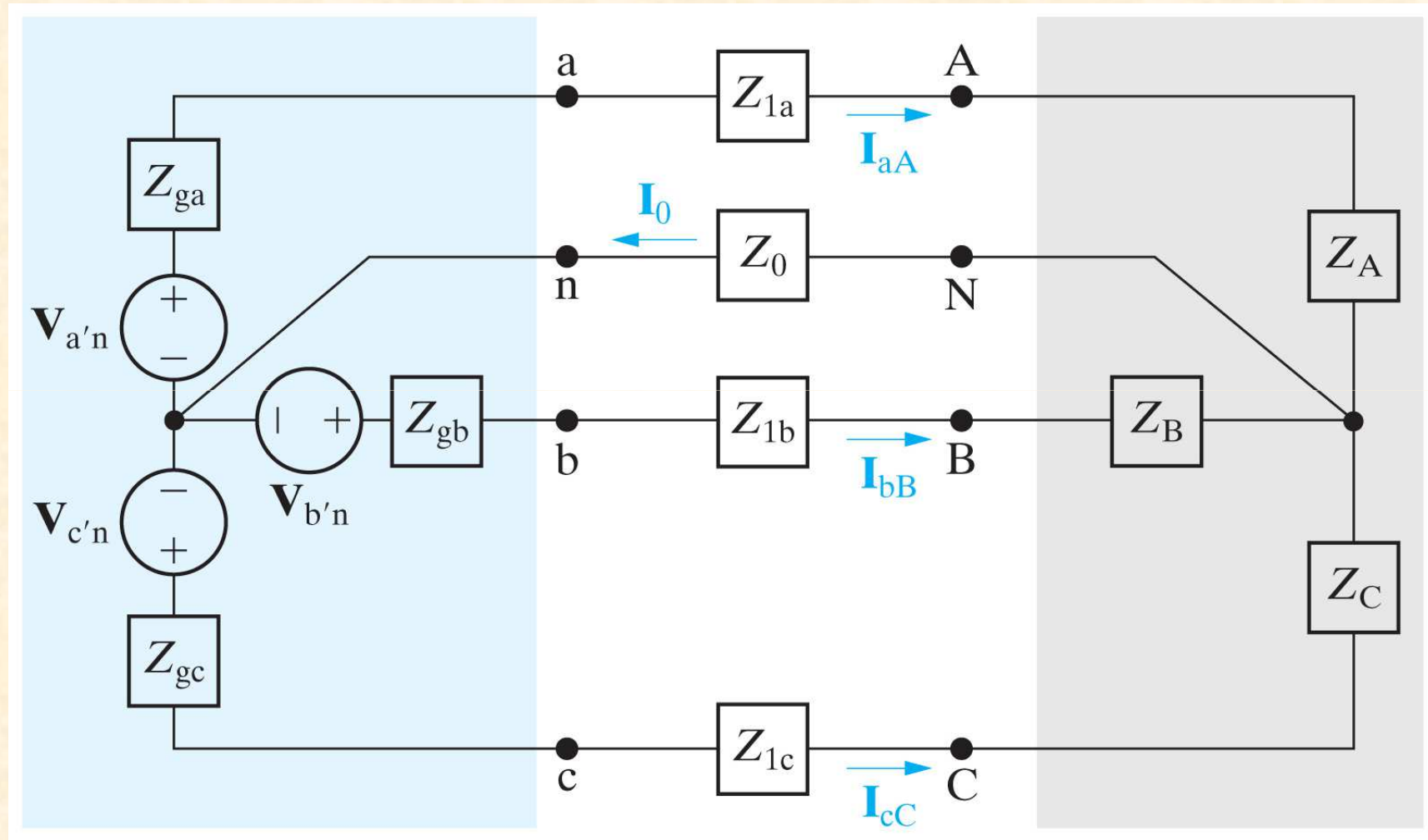

Y-Y Three-Phase System (Four Wire)

- Z_g represents the internal generator impedance per phase
- Z_l represents the impedance of the line connecting the generator to the load
- $Z_{A,B,C}$ represents the load impedance per phase
- Z_o represents the impedance of the neutral conductor



Neutral Voltage for Y-Y System

➤ Using source neutral as a reference, the Node-Voltage equation at node N can be written as:

$$\frac{\mathbf{V}_N}{Z_o} + \frac{\mathbf{V}_N - \mathbf{V}_{a'n}}{Z_A + Z_{la} + Z_{ga}} + \frac{\mathbf{V}_N - \mathbf{V}_{b'n}}{Z_B + Z_{lb} + Z_{gb}} + \frac{\mathbf{V}_N - \mathbf{V}_{c'n}}{Z_C + Z_{lc} + Z_{gc}} = 0.$$

➤ *For a balance three-phase system;*

✓ Three-phase voltages are balanced,

✓ $Z_{ga} = Z_{ga} = Z_{ga}$, $Z_{la} = Z_{la} = Z_{la}$ and $Z_A = Z_B = Z_C$

$$Z_{\phi} = Z_A + Z_{la} + Z_{ga}$$



Neutral Voltage for Y-Y System

➤ The neutral voltage can be given by:

$$\mathbf{V}_N \left(\frac{1}{Z_o} + \frac{3}{Z_\phi} \right) = \frac{\mathbf{V}_{a'n} + \mathbf{V}_{b'n} + \mathbf{V}_{c'n}}{Z_\phi}.$$

□ As the three-phase voltages are balanced (i.e. $\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$), therefore the neutral voltage must be equals zero

$$\mathbf{V}_N = 0.$$

